

EE214: Homework 1

Prateek Garg 20D070060

7th August 2021

For $M=0$, the circuit act as a 4-bit adder. For $M=1$, the circuit act as a subtractor.

B_i	M	$B_i \text{ XOR } M$
1	0	1
0	0	0
1	1	0
0	1	1

XOR Truth Table

For each B_i , if $M=0$ the output through XOR gate is B_i itself. So binary addition is done between A and B using full adders.

If $M=1$, the output through XOR gate is B_i' for each i. The final output S would be $A+B'$. Since 2's complement subtraction for two numbers X and Y is given by $X+Y'$, this clarifies that the subtraction has been performed by the circuit.